

TECHNOLOGICAL UNIVERSITY OF THE PHILIPPINES  
ELECTRONICS ENGINEERING DEPARTMENT

**ASSIGNMENT NO. 4**

CPET11 – BET-CPET-3A / 7:00 AM – 10:00 AM W

Submitted By:

Arenas, Joseph

Estrada, Cyrusz Adrienne

Gutierrez, Geo Kentzer

Pacis, Lian Gil

Recaña, Jordan

Submitted To:


Prof. Ralph Sherwin Corpuz

Faculty


1. Design an Arduino UNO interface using TinkerCAD. For each condition, show the schematic diagram, pictorial diagram, computations, and C++ program. The following are the requirements (100 points)

- Turn on 5 green LEDs for 5 seconds then turn off afterwards.

### Schematic Diagram:

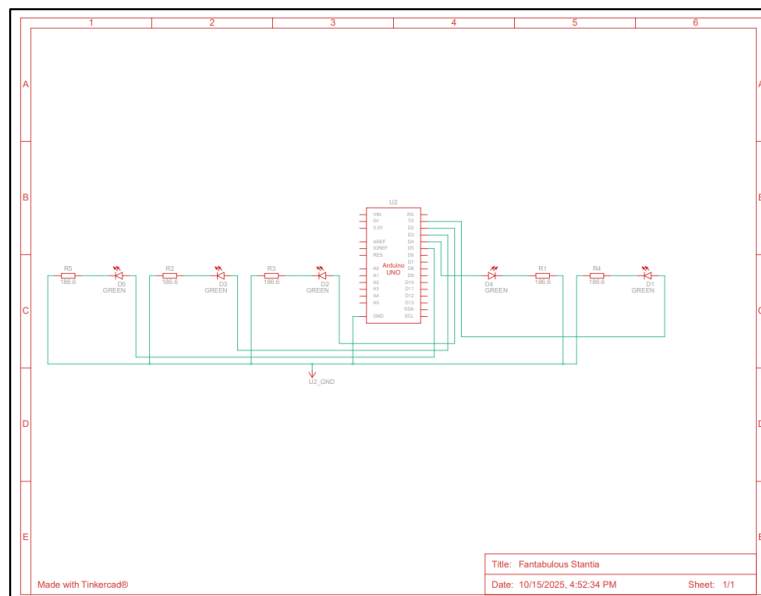

### Pictorial Diagram:

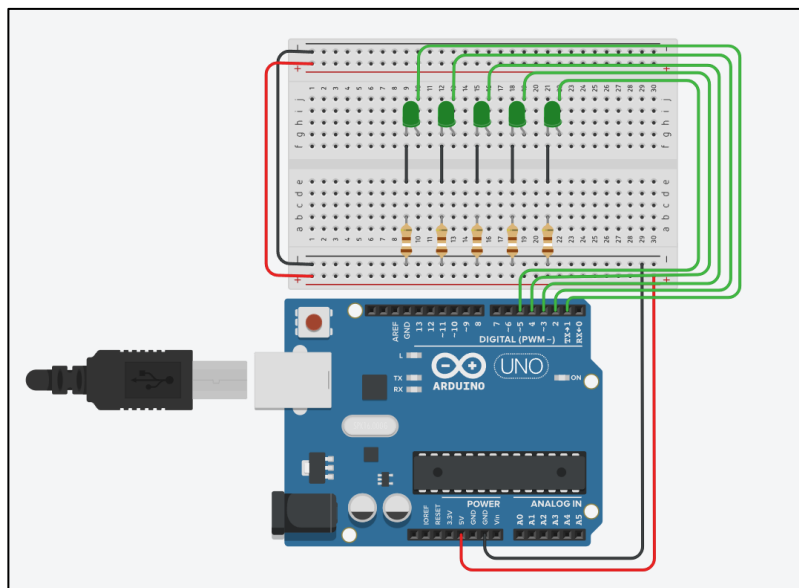

**Computation:**

$$R = V/I$$

$$R = V_{cc} - V_{led} / 15\text{mA}$$

$$R = 5 - 2.2 / 15 \text{ mA}$$

$$R = 186.6\Omega$$

**C++ Code:**

```
const int LED1 = 1;
const int LED2 = 2;
const int LED3 = 3;
const int LED4 = 4;
const int LED5 = 5;


void setup() {
  pinMode(LED1, OUTPUT);
  pinMode(LED2, OUTPUT);
  pinMode(LED3, OUTPUT);
  pinMode(LED4, OUTPUT);
  pinMode(LED5, OUTPUT);
}

void loop()
{
  digitalWrite(LED1, HIGH);
  digitalWrite(LED2, HIGH);
  digitalWrite(LED3, HIGH);
  digitalWrite(LED4, HIGH);
  digitalWrite(LED5, HIGH);
  delay(5000);


  digitalWrite(LED1, LOW);
  digitalWrite(LED2, LOW);
  digitalWrite(LED3, LOW);
  digitalWrite(LED4, LOW);
  digitalWrite(LED5, LOW);
  delay(5000);
  while (true);
}
```

- If pushbutton 1 is activated, 5 green LEDs will turn on for 2 seconds. Meanwhile, if pushbutton 2 is activated, 5 red LEDs will turn on for 5 seconds.

### Schematic Diagram:

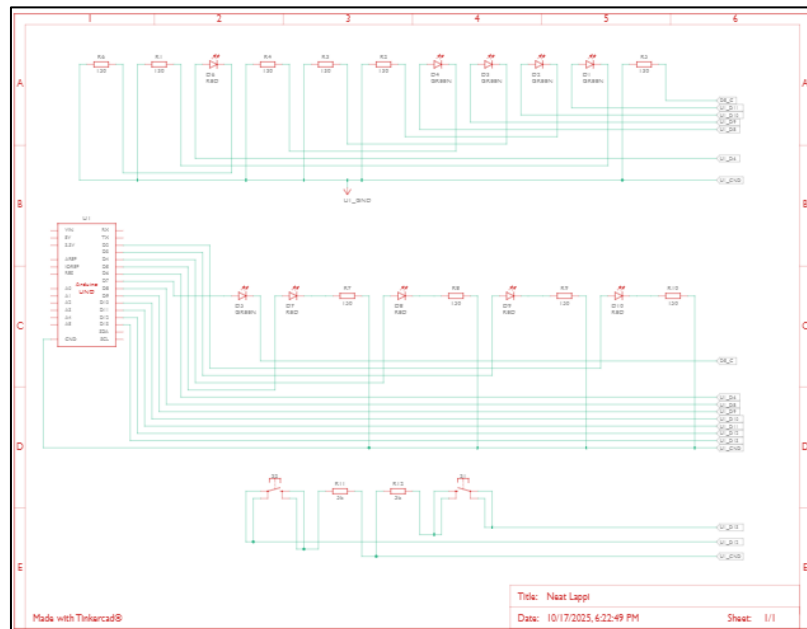

### Pictorial Diagram:

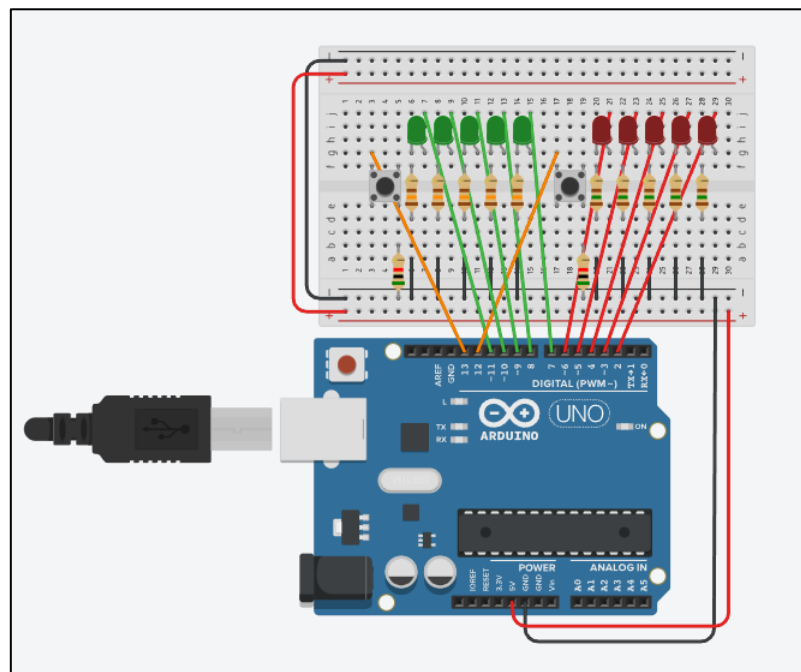

### Computations:

- **Limiting Resistor for each Red LED**

$$R = V/I$$

$$R = V_{cc} - V_{led} / 20\text{mA}$$

$$R = 5\text{V} - 2\text{V} / 20\text{ mA} = 3\text{V} / 20\text{mA}$$

$$R = 150\ \Omega$$

- **Limiting Resistor for each Green LED**

$$R = V/I$$

$$R = V_{cc} - V_{led} / 20\text{mA}$$

$$R = 5\text{V} - 2.41\text{V} / 20\text{ mA} = 2.59\text{V} / 20\text{mA}$$

$$R = 129.5\text{ or }130\Omega$$

- **Pull down Resistor for Push Button**

(1 mA is chosen as the desired current because it provides a strong enough pull to keep the input pin stable at LOW, while still being small enough to minimize power consumption and prevent unnecessary current flow when the button is pressed.)

$$R = V/I$$

$$R = V_{cc} / 1\text{ mA}$$

$$R = 5\text{V} / 1\text{ mA}$$

$$R = 5\text{k}\ \Omega$$

### C++ Program:

```
int ledNum = 10;
int ledPin[] = {2, 3, 4, 5, 6, 7, 8, 9, 10, 11};
int button1 = 13;
int button2 = 12;

void setup() {
  for (int x = 0; x < ledNum; x++) {
    pinMode(ledPin[x], OUTPUT);
  }
  pinMode(button1, INPUT_PULLUP);
  pinMode(button2, INPUT_PULLUP);
}


void loop() {
  int buttonState1 = digitalRead(button1);
  int buttonState2 = digitalRead(button2);
```

```
if (buttonState2 == LOW) {  
    digitalWrite(ledPin[0], HIGH);  
    digitalWrite(ledPin[1], HIGH);  
    digitalWrite(ledPin[2], HIGH);  
    digitalWrite(ledPin[3], HIGH);  
    digitalWrite(ledPin[4], HIGH);  
    delay(5000);  
    digitalWrite(ledPin[0], LOW);  
    digitalWrite(ledPin[1], LOW);  
    digitalWrite(ledPin[2], LOW);  
    digitalWrite(ledPin[3], LOW);  
    digitalWrite(ledPin[4], LOW);  
}
```


```
if (buttonState1 == LOW) {  
    digitalWrite(ledPin[5], HIGH);  
    digitalWrite(ledPin[6], HIGH);  
    digitalWrite(ledPin[7], HIGH);  
    digitalWrite(ledPin[8], HIGH);  
    digitalWrite(ledPin[9], HIGH);  
    delay(2000);  
    digitalWrite(ledPin[5], LOW);  
    digitalWrite(ledPin[6], LOW);  
    digitalWrite(ledPin[7], LOW);  
    digitalWrite(ledPin[8], LOW);  
    digitalWrite(ledPin[9], LOW);  
}  
}
```

- If pushbutton 1 is activated, 10 yellow LEDs will light in sequence (i.e., running lights from left to right). Meanwhile, if pushbutton 2 is activated these LEDs light up in reverse mode. There is a pull-down resistor used to minimize voltage fluctuation.

### Schematic Diagram:

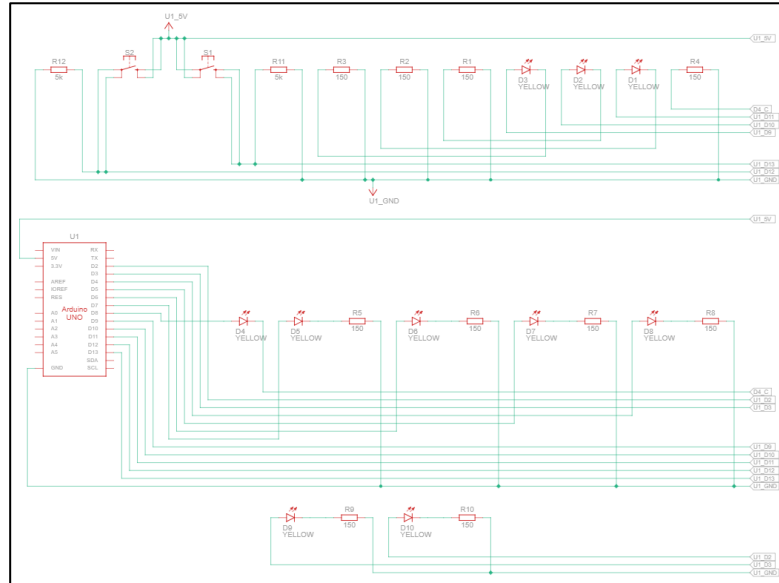

### Pictorial Diagram:

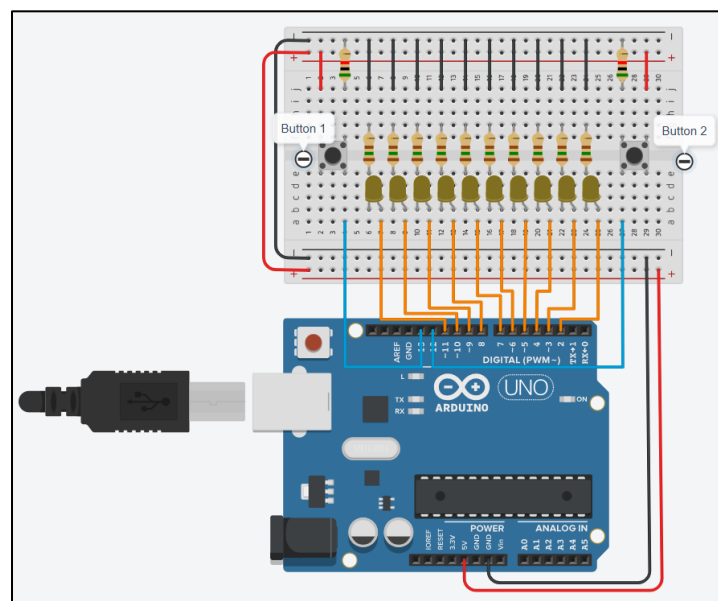

### Computations:

- **Limiting Resistor for each LED**

$$R = V/I$$

$$R = V_{cc} - V_{led} / 20\text{mA}$$

$$R = 5V - 2V / 20\text{ mA} = 3V / 20\text{mA}$$

$$R = 150\ \Omega$$

- **Pull down Resistor for Push Button**

(1 mA is chosen as the desired current because it provides a strong enough pull to keep the input pin stable at LOW, while still being small enough to minimize power consumption and prevent unnecessary current flow when the button is pressed.)

$$R = V/I$$

$$R = V_{cc} / 1\text{ mA}$$

$$R = 5V / 1\text{ mA}$$

$$R = 5\text{k}\ \Omega$$

### C++ Program:

```
const int numLEDs = 10;
int ledPins[numLEDs] = {11, 10, 9, 8, 7, 6, 5, 4, 3, 2};
int button1 = 13;
int button2 = 12;

void setup() {
  for (int i = 0; i < numLEDs; i++) {
    pinMode(ledPins[i], OUTPUT);
  }

  pinMode(button1, INPUT);
  pinMode(button2, INPUT);
}

void loop() {
  // Left-to-right sequence
  if (digitalRead(button1) == HIGH) {
    for (int i = 0; i < numLEDs; i++) {
      digitalWrite(ledPins[i], HIGH);
      delay(200);
      digitalWrite(ledPins[i], LOW);
    }
  }
}
```




```

// Right-to-left sequence
if (digitalRead(button2) == HIGH) {
  for (int i = numLEDs - 1; i >= 0; i--) {
    digitalWrite(ledPins[i], HIGH);
    delay(200);
    digitalWrite(ledPins[i], LOW);
  }
}
}
}


```

2. In reference to your proposed microcontroller application study, design the schematic diagram, pictorial diagram, computations, and C++ program. Simulate and take a video recording on the functional operation of the system (100 points)

### Schematic Diagram:

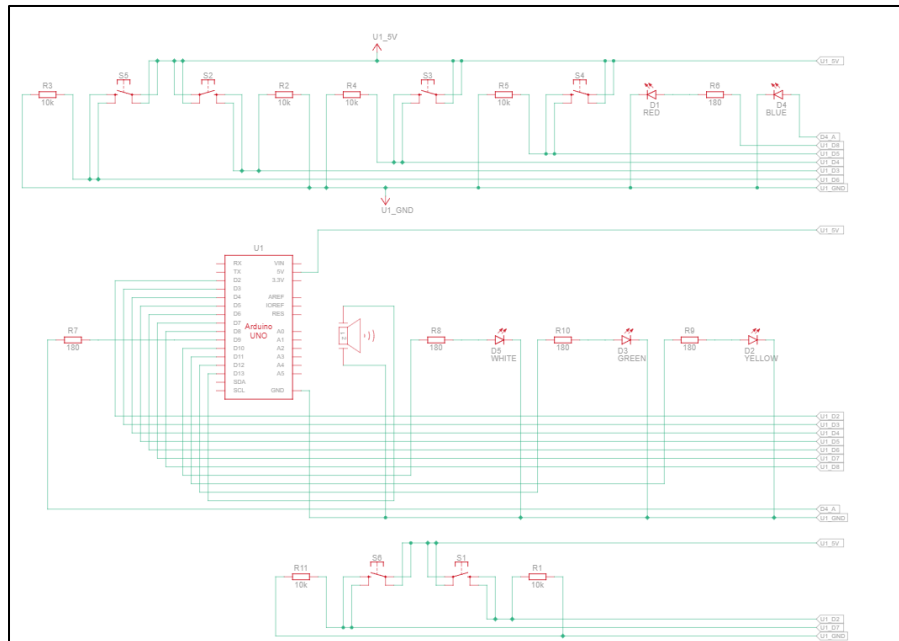

**Pictorial Diagram:**

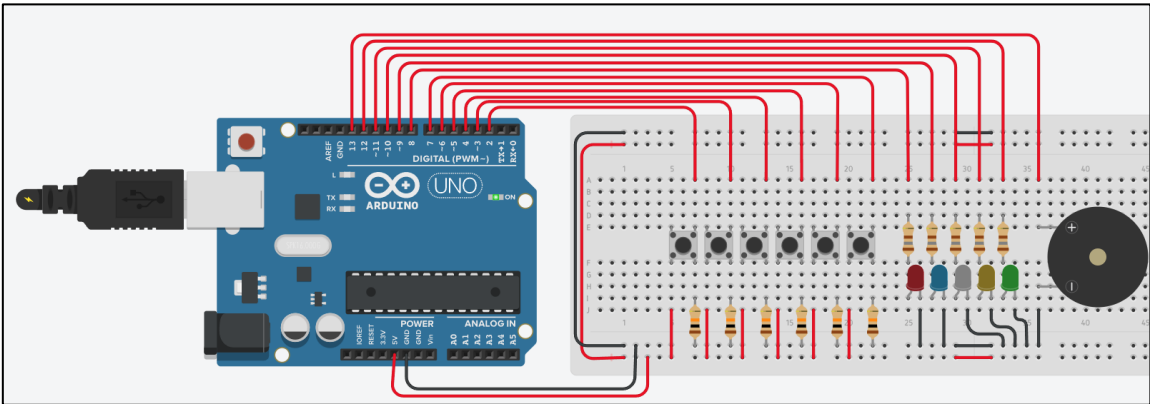

**Computations:**

This simple simulation system features a set of buttons, different color LEDs, resistors, 1 buzzer and an Arduino Uno Board. The 5 buttons represent the 5 sensors that will be used in the system, namely, Temperature (DS18B20), Humidity (DHT22), Smoke (MQ-2), Gas (MQ-9), Oxygen (ZE03-O2). These buttons will be represented by a set of LEDs and 1 buzzer. If the temperature button is pressed, a red colored LED will light, and the buzzer will go high (there will be different frequency per button (sensors) just for categorization). Lastly, there will be a main button wherein if pressed, will light up all the LEDs and turn on the buzzer (which signifies that all sensors sensed a change in the environment). Below is the representation of the simulation logic:

Buttons	Simulated Sensor	LED Color	Buzzer Tone
Button 1	Temperature (DS18B20)	Red	1000hz
Button 2	Humidity (DHT22)	Blue	800hz
Button 3	Smoke (MQ-2)	White	1200hz
Button 4	Gas (MQ-9)	Yellow	900hz
Button 5	Oxygen (ZE03-O2)	Green	2000hz
Button 6	All sensor	All LEDs	Default

Below is the pin connection of the various components to the Arduino Uno R3:

Component	Arduino Pin
Temperature Button	2
Humidity Button	3
Smoke Button	4
Gas Button	5
Oxygen Button	6
Main Button	7
Temperature LED (Red)	8
Humidity LED (Blue)	9
Smoke LED (White)	10
Gas LED (Yellow)	11
Oxygen LED (Green)	12

The following information is about the computations for the necessary components (resistor). Using the formula  $R = (V_{\text{supply}} - V_{\text{led}}) / I$  (required current of LED). We have calculated the necessary resistor value per led:

LED Color	$V_{\text{LED}}$	I	Computed R	Nearest Value
Red	2.0V	0.02A	$(5 \text{ V} - 2 \text{ V}) / 0.02 \text{ A} = 150 \Omega$	180 $\Omega$ or 220 $\Omega$
Yellow	2.1V	0.02A	$(5 - 2.1) / 0.02 = 145 \Omega$	180 $\Omega$ or 220 $\Omega$
Green	2.2V	0.02A	$(5 - 2.2) / 0.02 = 140 \Omega$	180 $\Omega$ or 220 $\Omega$
Blue	3.2V	0.02A	$(5 - 3.2) / 0.02 = 90 \Omega$	180 $\Omega$ or 220 $\Omega$

<b>White</b>	3.0V	0.02A	$(5 - 3.0)/0.02 = 100 \Omega$	180 $\Omega$ or 220 $\Omega$
--------------	------	-------	-------------------------------	------------------------------

### C++ Code:

```
// Define pins

const int buttonPins[5] = {2, 3, 4, 5, 6}; // Sensor buttons
const int ledPins[5] = {8, 9, 10, 11, 12}; // Sensor LEDs
const int mainButton = 7; // Main alarm button
const int buzzer = 13; // Single buzzer

// Frequencies for each sensor
const int frequencies[5] = {1000, 800, 1200, 900, 700};

void setup() {
  for (int i = 0; i < 5; i++) {
    pinMode(buttonPins[i], INPUT);
    pinMode(ledPins[i], OUTPUT);
  }
  pinMode(mainButton, INPUT);
  pinMode(buzzer, OUTPUT);
}

void loop() {
  // Main alarm button pressed?
  if (digitalRead(mainButton) == HIGH) {
    activateAllAlarms();
  } else {
    bool anyActive = false;
```

```

// Check each "sensor"
for (int i = 0; i < 5; i++) {
    if (digitalRead(buttonPins[i]) == HIGH) {
        digitalWrite(ledPins[i], HIGH);
        tone(buzzer, frequencies[i]); // Each has unique tone
        anyActive = true;
        delay(100); // Small delay for clarity
    } else {
        digitalWrite(ledPins[i], LOW);
    }
}

// Turn off buzzer if no buttons are pressed
if (!anyActive) {
    noTone(buzzer);
}

}

// Main alarm function
void activateAllAlarms() {
    // Turn all LEDs ON
    for (int i = 0; i < 5; i++) {
        digitalWrite(ledPins[i], HIGH);
    }

    // Strong general alarm sound
    tone(buzzer, 2000);
    delay(1000);
}

```

```

// Turn everything OFF

for (int i = 0; i < 5; i++) {
    digitalWrite(ledPins[i], LOW);
}

noTone(buzzer);
}

```

3. Specify the percentage contribution of each group member (100% total). Each member should sign to confirm the breakdown of contribution.


Contributions of each group member:

ARENAS, JOSEPH .....	20%
ESTRADA, CYRUS .....	20%
GUTIERREZ, GEO KENTZER .....	20%
PACIS, LIAN GIL .....	20%
RECAÑA, JORDAN .....	20%
<b>TOTAL</b> .....	<b>100%</b>


Signature of each group member:

A handwritten signature in black ink, featuring a large, stylized 'A' and 'J' that are connected, with a horizontal line extending from the end.


ARENAS, JOSEPH

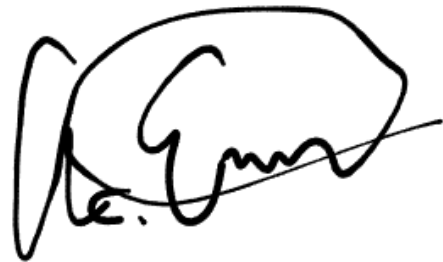A handwritten signature in black ink, featuring a large, stylized 'E' and 'C' that are connected, with a horizontal line extending from the end.

ESTRADA, CYRUZ

A handwritten signature in black ink, featuring a large, stylized 'G' and 'K' that are connected, with a horizontal line extending from the end.

GUTIERREZ, GEO KENTZER

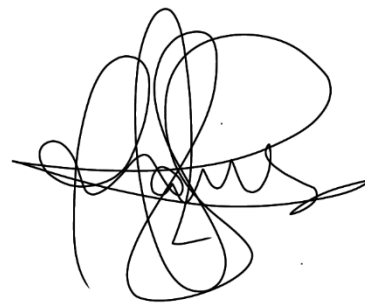A handwritten signature in black ink, featuring a large, stylized 'L' and 'G' that are connected, with a horizontal line extending from the end.

PACIS, LIAN GIL

A handwritten signature in black ink, featuring a large, stylized 'R' and 'J' that are connected, with a horizontal line extending from the end.

RECAÑA, JORDAN